

**II B. Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2016**  
**BASIC ELECTRONICS AND DEVICES**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70


- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **THREE** Questions from **Part-B**

**PART -A**

1. a) What are meant by N-type impurity in semiconductor? (3M)
- b) List the application of photodiode (4M)
- c) what are the advantages of bridge rectifier (4M)
- d) Derive the relationship between  $\alpha$  and  $\beta$  (4M)
- e) Write the difference between BJT and JFET (3M)
- f) Define feedback amplifier? How it classify (4M)

**PART -B**

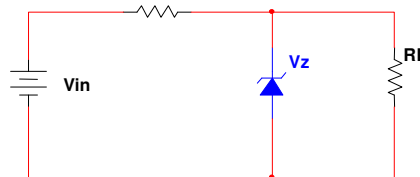2. a) Explain Hall Effect. How can Hall Effect be used to determine some of the properties of semiconductor? (8M)
- b) Prove that the conductivity of a semiconductor is given by,  $\sigma = q(P\mu_p + n\mu_n)$ . (8M)
3. a) Determine the range of input voltage that maintains the output voltage of 10V, for the regulator circuit shown  $r_R$  (8M)



- b) Explain characteristics of tunnel diode with the help of energy band diagrams (8M)
4. a) derive expressions for rectification efficiency, ripple factor, transformer utilization factor, form factor, peak factor of a half-wave rectifier with resistive load (8M)
- b) A full wave rectifier supplies a load requiring 300V at 200mA. Calculate the transformer secondary voltage for (8M)
  - (i) a capacitor input filter using a capacitor of 10mF, and (ii) a choke input filter using of 10H and a capacitor of 10 $\mu$ F. Neglect the resistance of choke
5. a) Explain how transistor is used as an amplifier (8M)
- b) Consider the self-bias circuit where  $V_{CC}=22.5V$ ,  $R_C=5.6\text{ k}\Omega$ ,  $R_2=10\text{ k}\Omega$  and  $R_1=90\text{ k}\Omega$ ,  $h_{FE}=55$ ,  $V_{BE}=0.6V$ . the transistor operates in active region. Determine (i) operating point (ii) stability factor (8M)
6. a) Explain principle of operation and characteristics of power IGBT (8M)
- b) Explain low frequency model of JFET (8M)
7. a) Why do need three RC networks for a phase shift oscillations? Can it be two or four? (6M)
- b) Draw the circuit diagram Push-full amplifiers and explain in detail (10M)

\*\*\*\*\*

|||||

**II B. Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2016**  
**BASIC ELECTRONICS AND DEVICES**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **THREE** Questions from **Part-B**

**PART -A**

1. a) What are meant by P-type impurity in semiconductor? (3M)
- b) List the application of LED (3M)
- c) compare full-wave rectifier and bridge rectifier (4M)
- d) What is Thermal runaway? How can it be avoid? (4M)
- e) Write the difference between JFET and MOSFET (4M)
- f) Write the application of power amplifier (4M)

**PART -B**

2. a) State and explain Mass-action Law (8M)
- b) Compute the conductivity of a silicon semiconductor which is doped with acceptor impurity to a density of  $10^{22}$  atoms/m<sup>3</sup>. Given that  $n_i = 1.4 \times 10^{16} / m^3$ ,  $\mu_n = 0.145 m^2 / V - s$  and  $\mu_p = 0.05 m^2 / V - s$ . (8M)
3. a) Explain V-I characteristics of a PN junction diode (8M)
- b) Design a zener regulator for the following specifications: output voltage,  $V_0=5V$ , load current,  $I_L = 20mA$ , input voltage,  $V_i = 12V \pm 3V$ , zener wattage,  $P_z=500mW$  (8M)
4. a) Derive expressions for rectification efficiency, ripple factor, transformer utilization factor, form factor, peak factor of a full-wave rectifier with resistive load (8M)
- b) compare the performance of inductive, L-section and  $\pi$ -section filters (8M)
5. a) Explain how transistor is used as an switch (8M)
- b) Derive an expression for the stability factor of a CB bias circuit (8M)
6. a) Explain principle of operation and characteristics of SCR (8M)
- b) Explain how JFET as an amplifier (8M)
7. a) Explain the operation of wein-bridge oscillator with the help of neat circuit diagram. How is amplitude stability achieved in this circuit? (8M)
- b) Explain the operation Class C power amplifier with neat circuit diagram and its efficiency (8M)

\*\*\*\*\*

**II B. Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2016**  
**BASIC ELECTRONICS AND DEVICES**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **THREE** Questions from **Part-B**
- ~~~~~

**PART -A**

1. a) Write the difference between intrinsic and extrinsic semiconductors (3M)
- b) Explain the formation of depletion region in a PN junction (4M)
- c) What is the need for filters in power supplies? (4M)
- d) What is the need for biasing a transistor? (3M)
- e) Write the application of JFET (4M)
- f) Write the Condition for oscillations (4M)

**PART -B**

2. a) Derive the conductivity equation for an N-type and P-type semiconductor (8M)
- b) The mobility of electrons and holes in a sample of intrinsic germanium at room temperature are  $0.36 \text{ m}^2/\text{V-s}$  and  $0.17 \text{ m}^2/\text{V-s}$ , respectively. If the electron and hole densities are each equal to  $2.5 \times 10^{19} / \text{m}^3$ , calculate the conductivity (8M)
3. a) Explain about Avalanche break down in detail (8M)
- b) In a Zener regulator, the D.C input is  $10\text{V} \pm 20\%$ , the output requirement are 5V, 20mA, Assume  $I_{z(\text{min})}$  and  $I_{z(\text{max})}$  as 5mA and 80mA respectively. Design the zener regulator (8M)
4. a) draw the circuit diagram of full-wave rectifier and explain its operation (8M)
- b) A bridge rectifier with capacitor filter is fed from 220V to 40V step-down transformer. If average d.c current is load is 1A and capacitor filter of  $800\mu\text{F}$ , calculate the load regulation and ripple factor, assume power line frequency of 50Hz. neglect diode forward resistance and d.c resistance of secondary of transformer (8M)
5. a) Determine the h-parameters from the characteristics of CB configuration (8M)
- b) Explain about Bias Compensation in transistor (8M)
6. a) Explain principle of operation and characteristics of thyristor (8M)
- b) Explain about enhancement and depletion mode of MOSFET (8M)
7. a) Draw the circuit diagram of RC phase shift oscillator .drive of expression for frequency of oscillations (8M)
- b) Explain the operation Class A power amplifier with neat circuit diagram (8M)

\*\*\*\*\*



**II B. Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2016**  
**BASIC ELECTRONICS AND DEVICES**  
 (Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is compulsory  
 3. Answer any **THREE** Questions from **Part-B**
- ~~~~~

**PART -A**

1. a) Define the terms conductivity and mobility in semiconductor (3M)
- b) Write the application of PN junction diode (4M)
- c) Compare half-wave and full-wave rectifier (4M)
- d) What is relation between  $I_B$ ,  $I_E$  and  $I_C$  in CB configuration? (4M)
- e) What is MOSFET? How many types of MOSFETs are their? (4M)
- f) Write the difference between the positive feedback and negative feedback amplifier (3M)

**PART -B**

2. a) Describe applications of Hall effect (8M)
- b) A crystal of pure germanium has sufficient antimony added to produce  $1.5 \times 10^{22}$  antimony atom/m<sup>3</sup>. the electron and hole mobility are  $0.38 \text{m}^2/\text{V-s}$  and  $0.18 \text{m}^2/\text{V-s}$  respectively, and the intrinsic charge density is  $2.5 \times 10^{19}/\text{m}^3$ . Calculate (i) the density of electrons and holes in crystal, and (ii) the conductivity. (8M)
3. a) Explain about Zener break down in detail (8M)
- b) Design a zener regulator for the following specifications: output voltage,  $V_0=5\text{V}$ , load current,  $I_L=20\text{mA}$ , input voltage,  $V_i=12\text{V} \pm 3\text{V}$ , zener wattage,  $P_z=500\text{mW}$  (8M)
4. a) A full-wave rectified voltage of 18V peak is applied across a  $500\mu\text{F}$  filter capacitor. Calculate the ripple and d.c voltages if the load takes a current of 100mA (8M)
- b) Determine the ripple factor of an L-type choke input filter comparing a 10H choke and  $8\mu\text{F}$  capacitor used with an full-wave rectifier. Compare with a simple  $8\mu\text{F}$  capacitor input filter at a load current of 50mA and also at 150mA. Assume the d.c voltage of 50V (8M)
5. a) Determine the h-parameters from the characteristics of CE configuration (8M)
- b) An NPN transistor if  $\beta=50$  is used in common emitter circuit with  $V_{cc}=10\text{V}$  and  $R_c=2\text{k}\Omega$ . the bias is obtained by connecting  $100\text{k}\Omega$  resistor from collector to base. Find the quiescent point and stability factor (8M)
6. a) Explain principle of operation and characteristics of power MOSFET (8M)
- b) Explain about JFET Characteristics (8M)
7. a) Draw the circuit diagram of Crystal oscillator .drive of expression for frequency of oscillations (8M)
- b) Find the efficiency of class A and class B of power amplifiers (8M)

\*\*\*\*\*

