

## TUTORIAL QUESTIONS

**Subject: Digital Logic Design**

Unit No.	Sl.No.	Questions	Bloom's Taxonomy level	Mapped with CO
<b>I</b>	1.	Convert (i) $(615.25)_8$ to $(?)_{10}$ , $(?)_2$ & $(?)_{16}$ . (ii) $(12.125)_{10}$ to $(?)_8$ , $(?)_2$ & $(?)_{16}$ . (iii) $(1101.111)_2$ to $(?)_{10}$ , $(?)_8$ & $(?)_{16}$ . (iv) $(6A5.B5)_{16}$ to $(?)_{10}$ , $(?)_2$ & $(?)_8$ .	3	CO 1
	2.	Solutions of quadratic equation $x^2 - 11x + 22 = 0$ are $x = 3$ & $x = 6$ $x = 3$ & $x = 6$ Identify the base of the system.	2	CO 1
	3.	Represent -45, +45, -65 & +65 in (i) sign magnitude form (ii) sign 1's complement form (iii) sign 2's complement form.	4	CO 1
	4.	Perform addition using Add and Subtract in BINARY (i) 1111 & 1010 (ii) 100100 & 10110	8	CO 1
	5.	Perform $28_{10} - (15)_{10}$ using 6-bit 2's complement subtraction.	5	CO 1
	6.	Perform (i) 5250-321 (ii) 3570-2100 (iii) 20-100 using 9's complement subtraction and 10's complement subtraction.	6	CO 1
	7.	Perform (i) $3250_{10} - 72532_{10}$ (ii) $72532_{10} - 3250_{10}$ using 10's complement subtraction and what did you infer from results.	7	CO 1
	8.	Perform arithmetic operations indicated below and verify answers if left most position is sign bit and negative numbers are in 2's complement form (i) $101011 + 111000$ (ii) $111001 - 001010$	9	CO 1
	9.	Perform (i) $3250_8 - 72532_8$ (ii) $72532_{10} - 3250_{10}$ using 7's complement subtraction and 16's complement subtraction. what did you infer from results.	7	CO 1
	10.	Perform (i) $3250_8 - 72532_8$ (ii) $72532_{10} - 3250_{10}$ using 1's complement subtraction and 10's complement subtraction.	10	CO 1
	11.	Convert 2's complement form and 2's complement form of subtraction with example.	1	CO 1
	12.	Convert 2's complement form and solve $3250_{10} - 72532_{10}$ .	8	CO 1
<b>II</b>		State basic Boolean theorems and properties and give proofs of each property and theorem.	2	CO 2
	2.	Prove that AND-OR network is equivalent to (i) NAND-NAND network and (ii) NOR-NOR network.	8	CO 2
	3.	Why universal gates? Why are they called so?	7	CO 2
	4.	Implement XOR & XNOR using Universal gates.	4	CO 2
	5.	Convert the following equations into standard sop $B, C, D = A'B + BC + CD' + ACD$ $B, C, D = (A + B' + C)(A + D)(B' + C')(A + B + C)$	5	CO 2
	6.	Convert the following equations into canonical pos	6	CO 2

		$B,C,D) = A'B + BC + CD' + ACD$ $B,C,D) = (A+B'+C)(A+D)(B'+C')(A+B+C)$		
	7.	Represent the following functions using (i) NAND gates (ii) NOR gates $F_1 = A(B+CD) + (BC)$ $F_2 = WX' + X'Y(Z+W')$	3	CO 2
	8.	Conclude $((AB)' + A' + AB)' = 0$	8	CO 2
	9.	Reduce the following Boolean expressions $AB'(C+BD) + A'B'A'B'C + (A+B+C')' + A'B'C'D$	9	CO 2
	10.	Write the complement of the following Boolean expressions $X'YZ + XZ$ $XY + X(WZ + WZ')$	10	CO 2
	11.	State the Demorgan's theorems and simplify the expression. $((AB)' + ABC)' + A(B + AB')'$	1	CO 2
	12.	Reduce $\{(CD)' + A\}' + A + CD + AB$ .	7	CO 2
III		Apply K-MAP (i) $f(a,b,c,d) = \sum(0,2,3,6,7) + d(8,10,11,15)$ (ii) $f(w,x,y,z) = \pi(4,5,6,7,8,12) \phi(1,2,3,9,11,14)$	5	CO 3
	2.	Apply K-MAP and implement using NAND gates (i) $f(a,b,c,d) = \sum(1,2,4,6,7,8,11,12,13)$ to POS form. (ii) $f(w,x,y,z) = \pi(1,3,7,11,15) \phi(0,2,5)$ to SOP form.	6	CO 3
	3.	Analyze $Y = \sum m(3,6,7,8,10,12,14,17,19,20,21,24,25,27,28)$ using K-Map method.	7	CO 3
	4.	Write minimal SOP and minimal POS expressions for the following function $F(A,B,C,D) = \sum m(0,1,1,5,8,9,10)$ .	9	CO 3
	5.	Solve the following Boolean expression using X-NOR and NOR gates $F = AB'CD' + A'BCD' + AB'C'D + A'BC'D$ .	10	CO 3
	6.	Consider K-MAP and simplify $f(a,b,c,d) = \sum(0,1,3,4,5,6,7,8,9,10,12,14)$ $f(a,b,c) = \pi(0,2,4,6)$	8	CO 3
	7.	Modify using K-MAP and implement using AOI logic $f(a,b,c,d) = \sum(1,2,4,6,7,8,11,12,13)$ to POS form. $f(w,x,y,z) = \pi(1,3,7,11,15) \phi(0,2,5)$ to SOP form	3	CO 3
	8.	Represent the following Boolean expression using X-OR and OR gates $F = AB'CD' + A'BCD' + AB'C'D + A'BC'D$ .	4	CO 3
	9.	Reproduce $Y = \sum(0,1,4,5,16,17,21,25,29)$ using K-Map method.	1	CO 3
	10.	Consider K-MAP simplification and implement using AOI logic $f(a,b,c,d) = \sum(1,2,4,12,13) + d(5,6,7)$ to POS form. $f(w,x,y,z) = \pi(1,3,9,11,15) \phi(0,2,5)$ to SOP form	8	CO 3
IV	1.	Design (i) HALF ADDER (ii) HALF SUBTRACTOR	9	CO 4

		(iii) FULL ADDER (iv) FULL SUBTRACTOR		
	2.	Explain 4 bit ripple adder/subtractor with suitable example.	7	CO 4
	3.	Design (i) 4bit magnitude comparator (ii) 5bit magnitude comparator	10	CO 4
	4.	Summarize the following code converters (i) GRAY-BINARY (ii) BINARY-BCD (iii) BCD-XS3 (iv) XS3-BINARY (v) INARY-GRAY	8	CO 4
	5.	Design (i) octal to binary encoder (ii) 4 bit priority encoder	9	CO 4
	6.	Reproduce HALF SUBTRACTOR and FULL ADDER using (i) MUX (ii) DEMUX (iii) DECODER	2	CO 4
	7.	Apply decoder and external gates for following (i) $F_1 = X'Y'Z' + XZ$ $F_2 = XY'Z' + X'Y$ $F_3 = X'Y'Z' + XY$ (ii) $F_1 = \sum(0,1,3,6,7)$ $F_2 = \sum(0,2,4,7)$	5	CO 4
	8.	Represent following using LOGIC GATE (i) 3 to 8 decoder (ii) 4 to 16 mux (iii) 1x16 demux	4	CO 4
	9.	Analyze following using (i) 4 input mux (ii) 8x1 mux (iii) 3 to 8 decoder (iv) 2 to 4 decoder $F_1 = \sum(0,1,3,6,7)$	7	CO 4
	10.	Apply (i) 4 input mux (ii) 8x1 mux (iii) 16x1 mux for following $F_1 = \sum(0,1,3,4,8,9,15)$	6	CO 4
	11.	Convert 4 to 16 decoder into demux	3	CO 4
V		Explain the operation of (a) SR latch using NOR gates (b) Gated D latch using NAND gates	7	CO5
	2.	Explain the operation of negative edge triggered D flip-flop when CP=1.	7	CO5
	3.	What is RACE AROUND condition? How can we eliminate it? Explain MASTER SLAVE JK flip-flop and state its advantages.	2	CO5
	4.	Explain the operation of positive edge triggered JK flip-flop in detail.	3	CO5
	5.	Distinguish combinational & sequential logic circuits?	8	CO5
	6.	List different methods used to trigger a flip-flop?	6	CO5
	7.	What is a flip-flop? Design basic flip-flop circuit with NAND gates.	1	CO5
	8.	Draw EXCITATION tables and TRUTH tables of (a) D (b) T (c) JK (d) SR flip-flops.	10	CO5

	9.	Write characteristic equations of (a) D (b) T (c) JK (d) SR flip-flops.	5	CO5
	10.	Define the following terms with respect to flip-flops (a) Setup time (b) Hold time (c) Propagation delay (d) Preset (e) Clear (f) Latch	8	CO5
	11.	Convert the following flip-flops (a) JK to D (b) T to D (c) D to SR (d) SR to JK (e) T to SR	4	CO5
VI		Distinguish Asynchronous & Synchronous sequential logic circuits?	8	CO6
	2.	Draw timing diagram explain operation of (a) 3 bit universal shift register. (b) 4 bit controlled buffer register.	7	CO6
	3.	Design Johnson's counter using a 2 bit shift register. Draw waveforms and list applications of shift register.	5	CO6
	4.	Explain about parallel in serial out shift register. How to load data word ABCD=1101 in the 4 bit bidirectional shift register in shift left mode.	2	CO6
	5.	Design a register for left & right shift of data for 10110101.	9	CO6
	6.	Explain about ring counter and twisted ring counter. Draw and explain about 4 bit ring counter.	8	CO6
	7.	Explain about synchronous ripple counter and compare merits and demerits.	3	CO6
	8.	Explain about 4 bit ripple down counter using positive edge triggered flip-flop.	4	CO6
	9.	Design ripple counter. Design BCD ripple counter.	1	CO6
	10.	Explain about working of 4 bit asynchronous counter.	7	CO6
	11.	Design (a) mod-12 synchronous up counter using 'T' flip-flop. (b) mod-10 synchronous down counter using 'JK' flip-flop. (c) mod-6 synchronous up counter using 'D' flip-flop. (d) mod-6 synchronous down counter using 'SR' flip-flop.	10	CO6
	12.	A counter has 14 stable states 0000 to 1101. If input frequency is 50KHz Compute its output frequency?	6	CO6



## **TUTORIAL QUESTIONS**

**Subject: Computer Graphics**

	UNIT – I	Blooms taxonomy	Mapping with outcome
1	Explain the Bresenham’s line drawing algorithm	4	CO2
2	Explain the midpoint circle drawing algorithm. Assume 10cm as the radius and co-ordinate origin as the center of the circle	4	
3	Explain (a) random and raster scan devices (b) primitives used for filling	3	
4	Explain about filled area primitives	3	
5	Explain D viewing pipeline in detail	3	
6	Explain Cohen-Sutherland’s line clipping algorithm.	4	
7	Derive the viewing Transformation matrix in detail	6	
8	Explain polygon clipping algorithm	3	
9	Explain the different 2D transformations	4	
10	Explain the about the lines of attribute primitives?	3	
UNIT – II			
1	Explain about parallel and perspective projection in detail?	9	CO2
2	Discuss the concept of three dimensional object representations?	8	
3	Explain curved line and splines	9	
4	Explain about quadric surface in detail?	9	
5	Discuss about the concept of Visualization of data sets?	7	
6	Explain about 3D Transformation in detail?	3	
7	Explain the concept of 3D viewing in detail?	4	
8	What are the methods of visible surface detection?	2	
9	What is back face detection ?give one example	1	
10	Write the concept of painter’s method?	1	
UNIT – III			
1	What is the importance of graphics programming?	2	CO3
2	Write short note on the following color models: I. RGB II. YIQ III. CMY IV. HSV	2	
3	What is computer animation? give one example	1	
4	Explain about general computer animation techniques?	3	
5	Discuss about raster animation in detail?	9	
6	Discuss about key frame systems?	4	
7	What are basic graphics primitives?	2	
8	Write the concept of drawing three dimensional objects?	2	
9	Write the concept of drawing three dimensional scenes?	2	
10	What is animation sequence?	2	
UNIT – IV			
1	What is rendering? give one example	1	
2	What is shading ?give one example	1	
3	Explain the concept of shading models?	4	
4	Discuss the concept of flat and smooth shading?	7	
5	Write the concept of adding textures to faces?	2	

6	Write the concept of adding shadows of objects?	9	CO4
7	Discuss about the concept of building a camera in a program?	9	
8	Explain the concept of creating shaded objects?	3	
9	Discuss about rendering textures?	3	
10	Discuss about drawing shadows?	2	
UNIT – V			
1	Discuss about the concept of Fractals and self similarity?	3	CO5
2	Explain about the concept of peano curves?	9	
3	What is creating image by iterated functions?	2	
4	What are Mandelbrot sets? Give example?	4	
5	Explain about Julia sets? Give example?	3	
6	Explain about Random Fractals? Give example?	4	
UNIT – VI			
1	What is meant by intersecting rays?	2	CO6
2	Give the relationship between intersecting rays and primitives?	2	
3	Write the concept of adding surface textures?	9	
4	What is reflection and transference?	2	
5	Write the concept of Boolean operation on objects?	2	