


Star To Delta Conversion Formula (Delta to Wye)

Three branches in an electrical network can be connected in numbers of forms but most common among them is either star or delta form. In delta connection, three branches are so connected, that they form a closed loop. As these three branches are connected nose to tail, they form a triangular closed loop, this configuration is referred as delta connection. On the other hand, when either terminal of three branches is connected to a common point to form a Y like pattern is known as star connection. But these star and delta connections can be transformed from one form to another. For simplifying complex network, delta to star or **star to delta transformation** is often required.

Delta To Star Conversion

The replacement of delta or mesh by equivalent star connection is known as **delta – star transformation**. The two connections are equivalent or identical to each other if the impedance is measured between any pair of lines. That means, the value of impedance will be the same if it is measured between any pair of lines irrespective of whether the delta is connected between the lines or its equivalent star is connected between that lines.

DELTA AND STAR CONNECTED RESISTORS

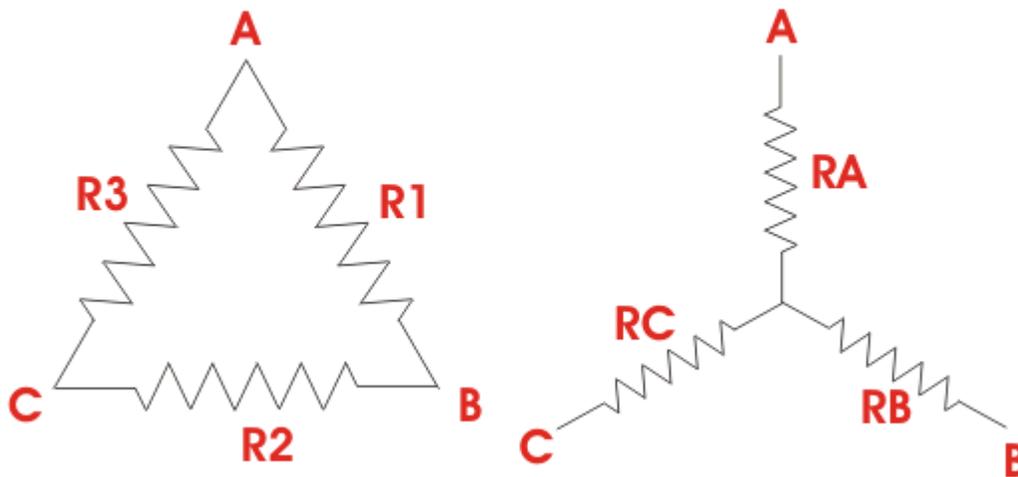

Consider a delta system that's three corner points are A, B and C as shown in the figure.

Electrical resistance of the branch between points A and B, B and C and C and A are R_1 , R_2 and R_3 respectively.

The resistance between the points A and B will be,

$$R_{AB} = R_1 || (R_2 + R_3) = \frac{R_1 \cdot (R_2 + R_3)}{R_1 + R_2 + R_3}$$

Now, one star system is connected to these points A, B, and C as shown in the figure. Three arms R_A , R_B and R_C of the star system are connected with A, B and C respectively. Now if we measure the resistance value between points A and B, we will get,

$$R_{AB} = R_A + R_B$$

Since the two systems are identical, resistance measured between terminals A and B in both systems must be equal.

$$R_A + R_B = \frac{R_1 \cdot (R_2 + R_3)}{R_1 + R_2 + R_3} \dots\dots\dots(i)$$

Similarly, resistance between points B and C being equal in the two systems,

$$R_B + R_C = \frac{R_2 \cdot (R_3 + R_1)}{R_1 + R_2 + R_3} \dots\dots\dots(ii)$$

And resistance between points C and A being equal in the two systems,

$$R_C + R_A = \frac{R_3 \cdot (R_1 + R_2)}{R_1 + R_2 + R_3} \dots\dots\dots(iii)$$

Adding equations (I), (II) and (III) we get,

$$2(R_A + R_B + R_C) = \frac{2(R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1)}{R_1 + R_2 + R_3}$$

$$R_A + R_B + R_C = \frac{R_1 \cdot R_2 + R_2 \cdot R_3 + R_3 \cdot R_1}{R_1 + R_2 + R_3} \dots\dots\dots(iv)$$

Subtracting equations (I), (II) and (III) from equation (IV) we get,

$$R_A = \frac{R_3 \cdot R_1}{R_1 + R_2 + R_3} \dots\dots\dots(v)$$

$$R_B = \frac{R_1 \cdot R_2}{R_1 + R_2 + R_3} \dots\dots\dots(vi)$$

$$R_C = \frac{R_2 \cdot R_3}{R_1 + R_2 + R_3} \dots\dots\dots(vii)$$

The relation of delta – star transformation can be expressed as follows.

The equivalent star resistance connected to a given terminal, is equal to the product of the two delta resistances connected to the same terminal divided by the sum of the delta connected resistances.

If the delta connected system has same resistance R at its three sides then equivalent star resistance r will be,

$$r = \frac{R \cdot R}{R + R + R} = \frac{R}{3}$$

Star To Delta Conversion

For **star – delta transformation** we just multiply equations (v), (VI) and (VI), (VII) and (VII), (V) that is by doing (v) × (VI) + (VI) × (VII) + (VII) × (V) we get,

$$R_A R_B + R_B R_C + R_C R_A = \frac{R_1 \cdot R_2^2 \cdot R_3 + R_1 \cdot R_2 \cdot R_3^2 + R_1^2 \cdot R_2 \cdot R_3}{(R_1 + R_2 + R_3)^2}$$

$$= \frac{R_1 \cdot R_2 \cdot R_3 (R_1 + R_2 + R_3)}{(R_1 + R_2 + R_3)^2}$$

$$= \frac{R_1 \cdot R_2 \cdot R_3}{R_1 + R_2 + R_3} \dots\dots\dots (viii)$$

Now dividing equation (VIII) by equations (V), (VI) and equations (VII) separately we get,

$$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

$$R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

$$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$